

# PHYSICS PRACTICAL SHEETS

Date: 20/08/2019

Prime CAMPUS

Class: BSC CSIT

Experiment No.: 3

Roll No.:

Group:

Shift: Morning

Sub.:

Object of the Experiment (Block Letter)

Set:

TO DESIGN AND STUDY THE SERIES LCR FINDING THE QUALITY FACTOR OF THE ELEMENTS.

## APPARATUS REQUIRED:

- |                              |                                                   |
|------------------------------|---------------------------------------------------|
| i) An inductor               | v) Capacitor                                      |
| ii) Resistor connecting wire | vi) An audio frequency oscillator (10KHz - 10MHz) |
| iii) Voltmeter               | vii) One way key                                  |
| iv) Ammeter                  |                                                   |

## THEORY:

When the resistor (R), inductor (L) & capacitor (C) are connected in series with a source of emf 'E', the circuit is called series resonance circuit as shown in fig (1).

Under certain conditions, the voltage and current are in phase, even though the circuit consists of L, C & R, the circuit behaves as a pure resistor. This phenomenon is called resonance. This occurs at single frequency known as resonance frequency ( $f_r$ ). At this frequency, the capacitive reactance ( $X_c = \frac{1}{\omega c}$ ) and inductive reactance ( $X_L = \omega L$ )

are equal and opposite, i.e.  $\frac{1}{\omega c} = \omega L \Rightarrow \omega^2 = \frac{1}{LC}$

$$\text{or, } \omega = \frac{1}{\sqrt{LC}} \Rightarrow 2\pi f = \frac{1}{\sqrt{LC}} \Rightarrow \boxed{f = \frac{1}{2\pi\sqrt{LC}}} \quad (1)$$

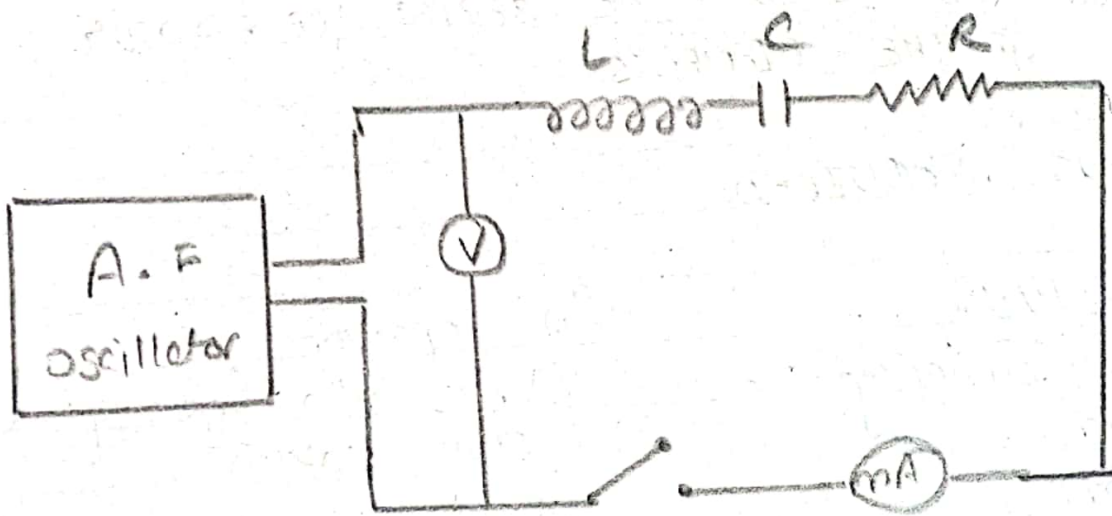


Fig (i) Series LC circuit

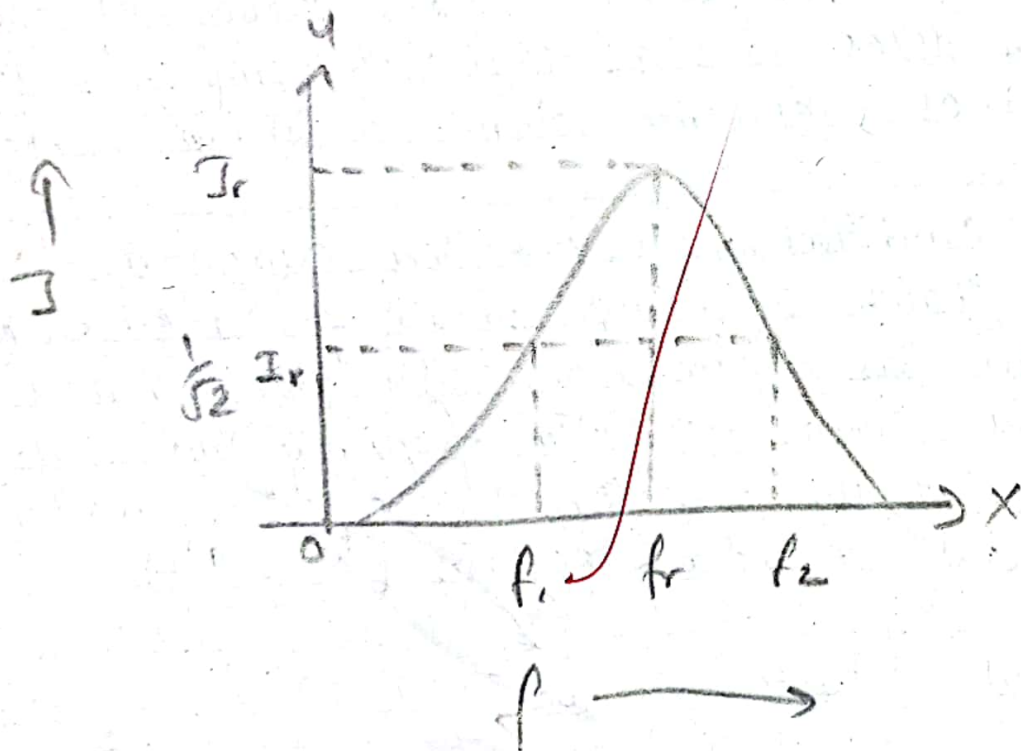


Fig (ii) graph of 'I' vs 'f'

The Quality factor of series LCR circuit is given by:

$$Q = \frac{2\pi f_r}{f_2 - f_1} \quad \text{--- (ii)}$$

where  $f_2$  &  $f_1$  are the values of frequency above & below the resonant frequency for which the current in the circuit is  $\frac{I_r}{\sqrt{2}} = 0.707 I_r$ , where  $I_r$  is current at resonance which is obtained by plotting a graph of current (I) vs frequency (f) as shown in fig. (ii).

### OBSERVATION:

Inductance (L) = 1.1 mH

Resistance (R) = 100- $\Omega$ , 200- $\Omega$  & 470- $\Omega$

Capacitance (C) = 0.22  $\mu$ F

LC of voltmeter = 0.2V

LC of ammeter = 0.2A

### Observation Table for measurement of current

SN	frequency (f) in kHz	Current in mA		
		$R_1 = 100\text{-}\Omega$	$R_2 = 200\text{-}\Omega$	$R_3 = 470\text{-}\Omega$
1	1	1.8	1.8	1.2
2	2	3.8	2.8	1.4
3	3	5.2	3.2	1.4
4	4	4.4	2.6	1.6
5	5	3.6	2.4	1.4
6	6	3.2	2.2	1.4

7	7	2.8	2	1.2
8	8	2.4	1.8	1.2
9	9	2.2	1.6	1.2
10	10	2	1.6	1

### CALCULATION:

From the graph, we can see that  
Resonant frequency ( $f_r$ ) = 3 kHz

$$f_1 = 1.9 \text{ kHz}$$

$$f_2 = 5 \text{ kHz}$$

Now,

$$\begin{aligned} \text{Quality factor (Q)} &= \frac{2\pi f_r}{f_2 - f_1} \\ &= \frac{2 \times 3.14 \times 3}{5 - 1.9} \\ &= 6.077 \end{aligned}$$

### RESULT:

The quality factor of the element of LCR circuit is found to be 6.077.

### CONCLUSION:

By the help of graph, the quality factor of the elements of LCR circuit can be found which is 6.077.

## PRECAUTIONS:

- i) The wires should be connected in correct places.
- ii) The apparatus should be handled properly.
- iii) The measurements must be taken properly.

